

# **FUNDAMENTALS OF ELECTRICITY AND ELECTRONICS**

**BHAVAT NGAMDEEVILAISAK**

# Voltage

**“The potential difference between two points”**




Independent  
voltage source

IDEAL SOURCES




Dependent  
voltage source

# Voltage “Measured in Volts (V)”

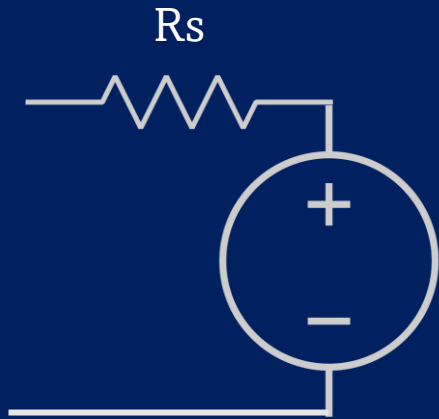

Independent  
voltage source

## PRACTICAL SOURCES

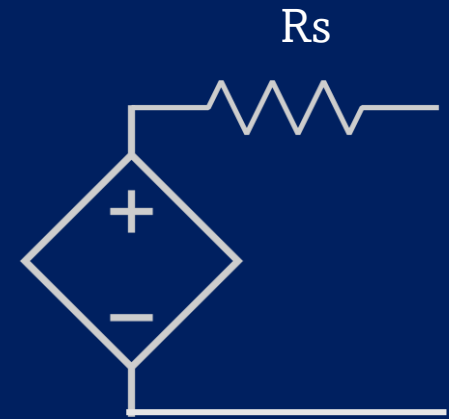

Dependent  
voltage source

# Current

**“An amount of charges flow through a cross section of conductor per amount of time”**




Independent  
current source

IDEAL SOURCES




Dependent  
current source

# Current “Measured in Ampere (A)”

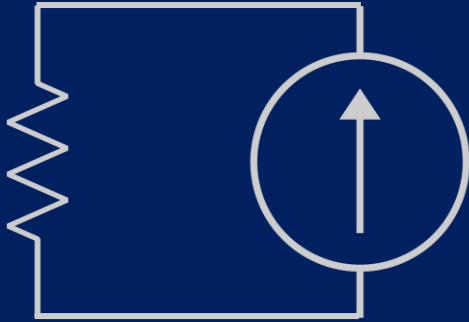

Independent  
current source

PRACTICAL SOURCES

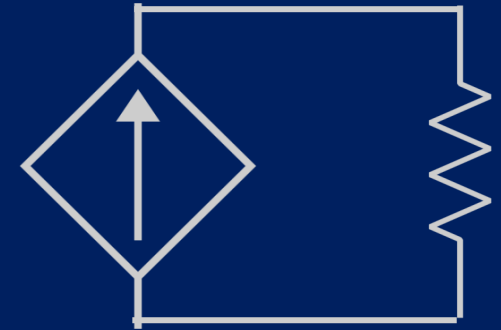


Dependent  
current source


# Resistance

**“An ability to resists the flow of current measured in Ohm ( $\Omega$ )”**





# Resistor Color Code

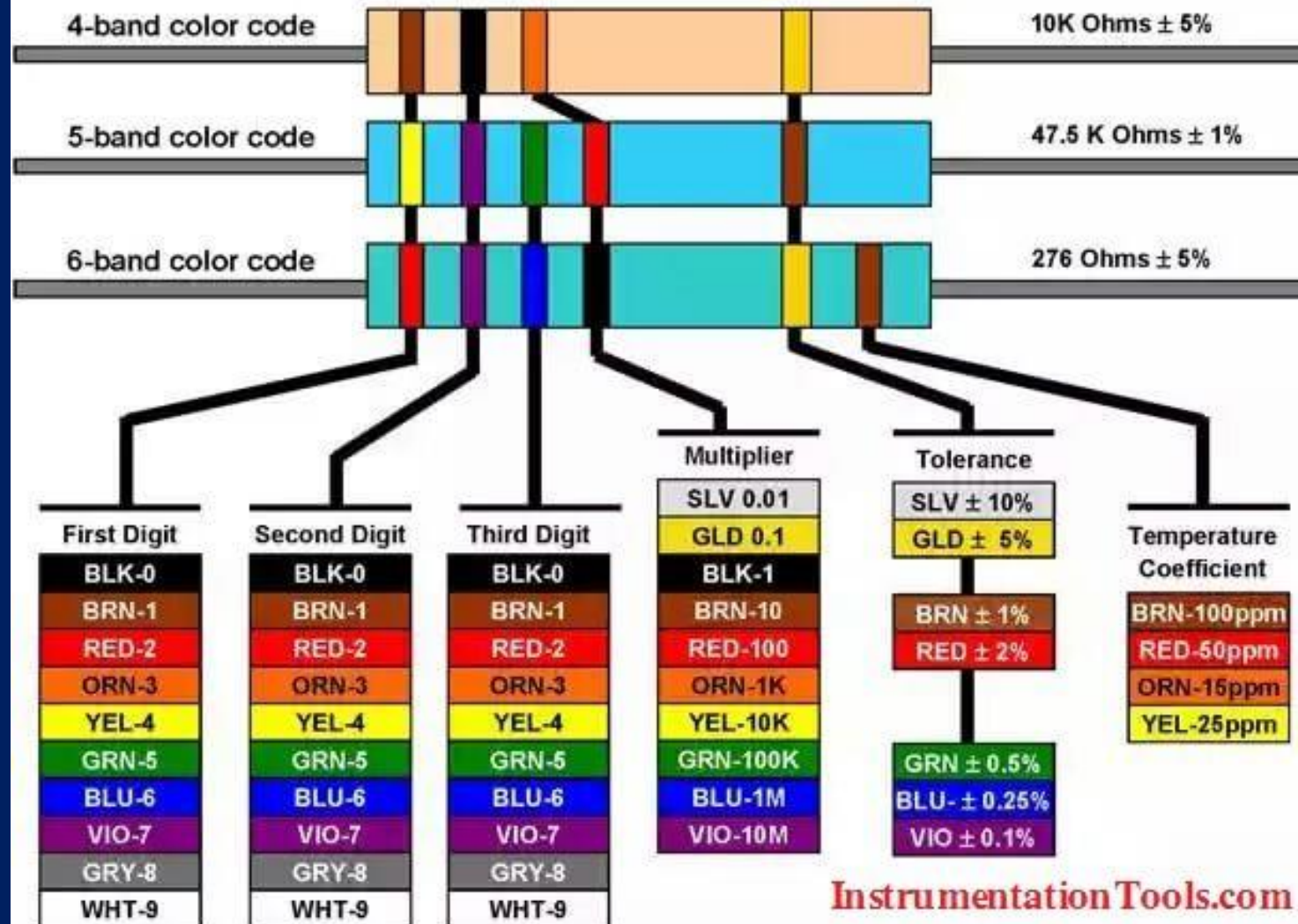

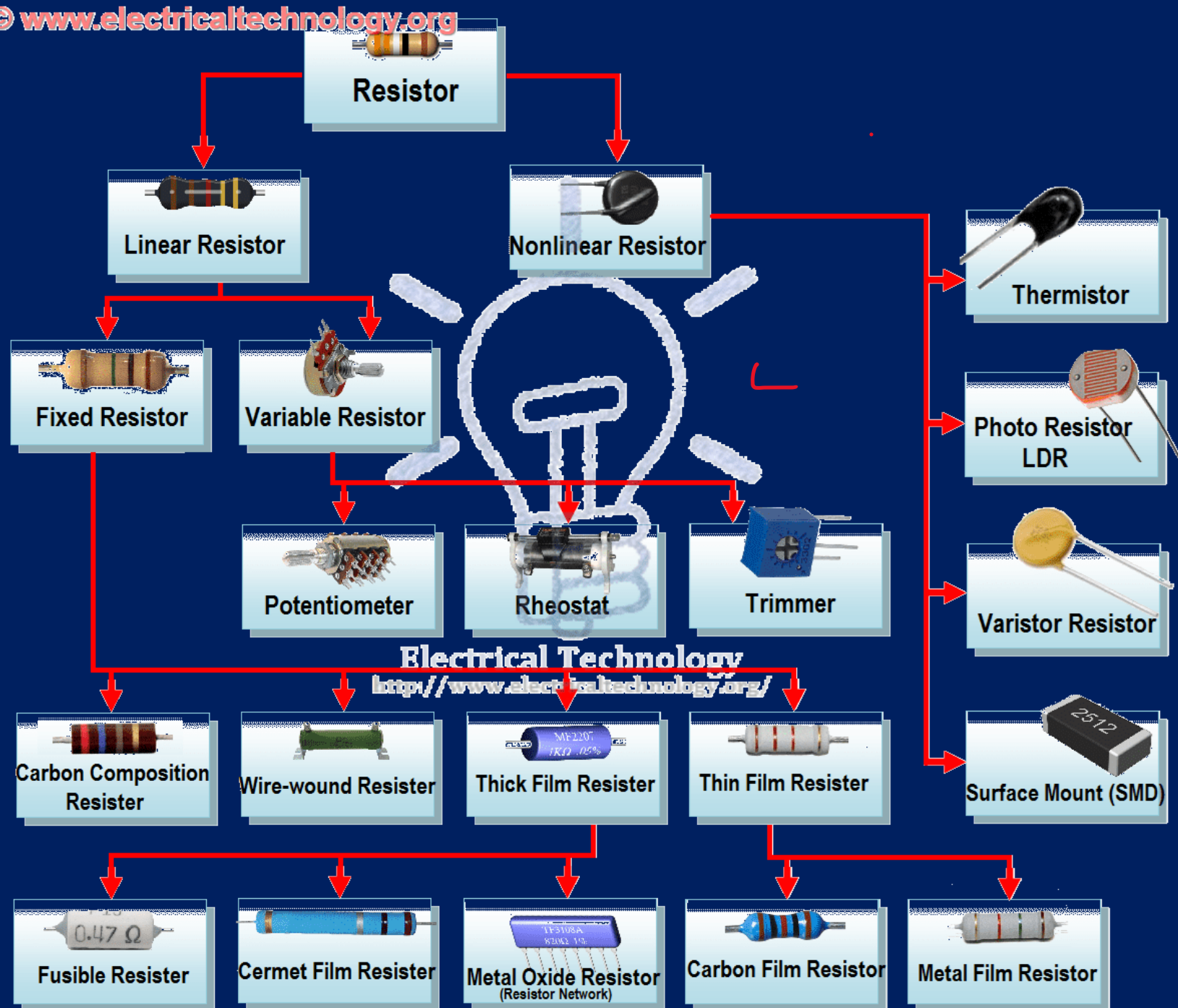





# Potentiometer

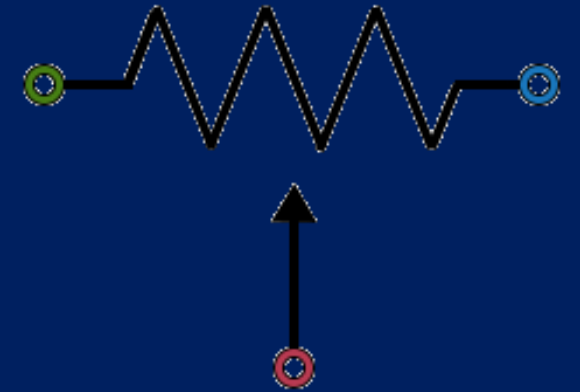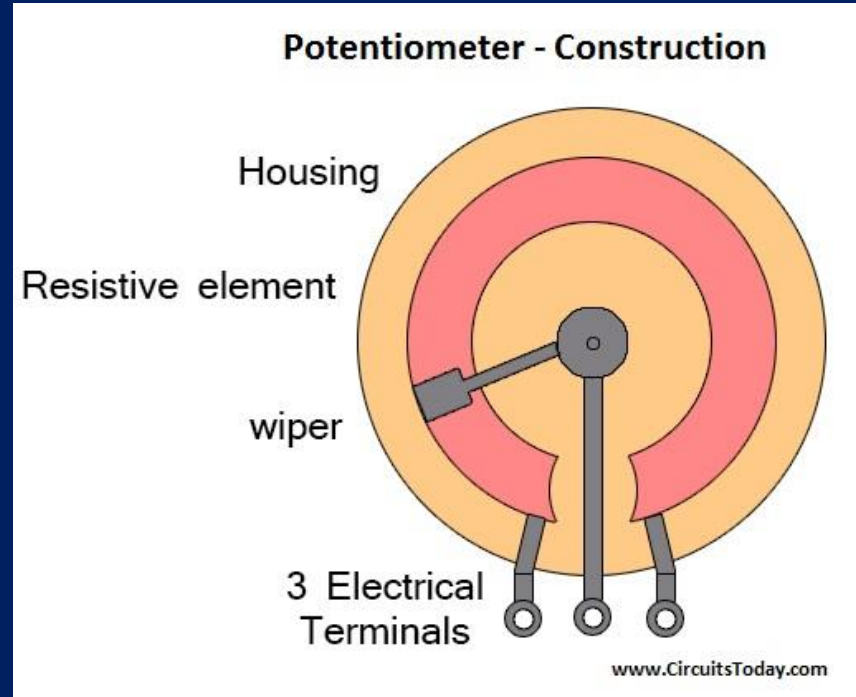


# Signal fundamentals

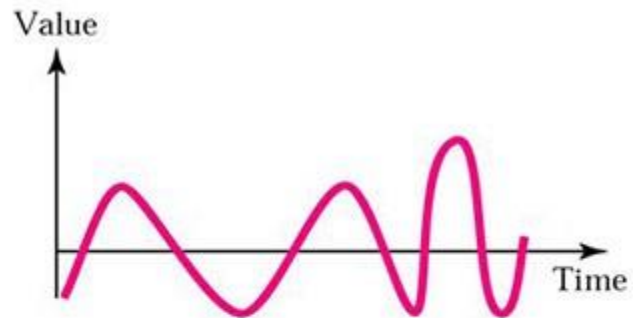


Analog signal

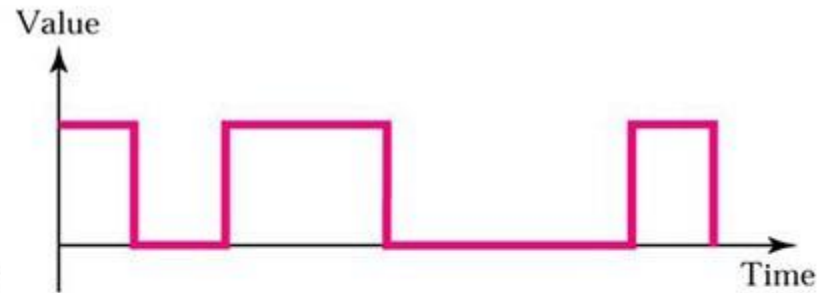

Digital signal

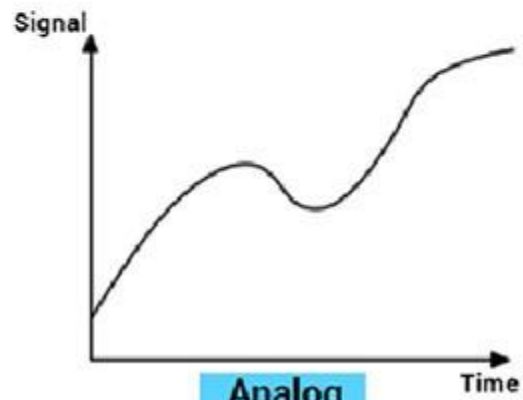

Analog

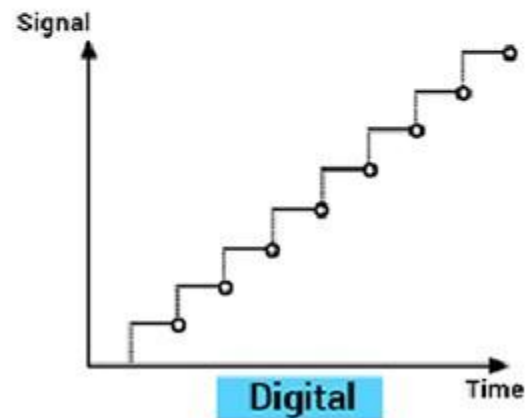

Digital


**Power** “The time rate of expending or absorbing energy measured in Watt (W)”



Passive sign convention  
(Absorb power)



Active sign convention  
(Deliver power)

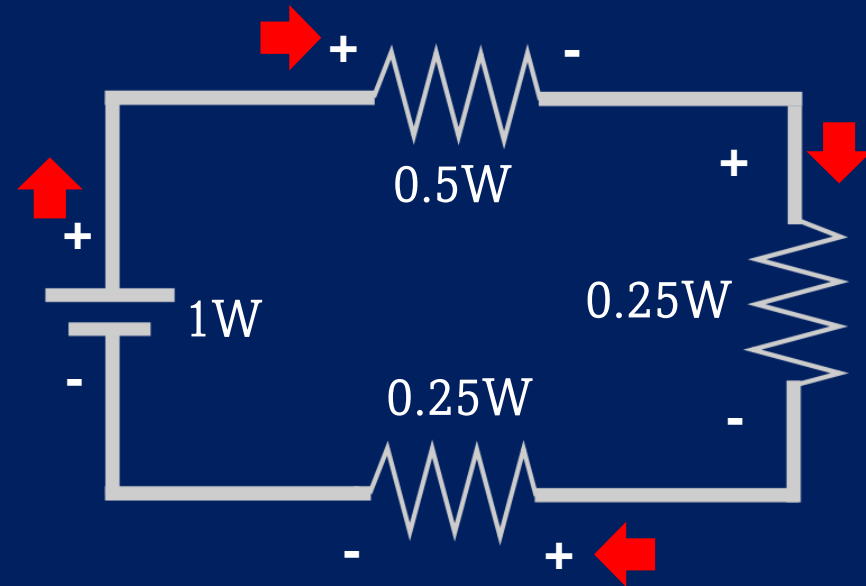

Absorb power = -(Deliver power)


## Unit transformation you should know

1. Current = Charge / Time :  $I = \frac{C}{s}$


2. Power = Energy / Time :  $P = \frac{J}{s}$

3. Conductance = 1 / Resistance :  $\mathcal{U} \text{ or } S = \frac{1}{R}$

# Ohm's Law

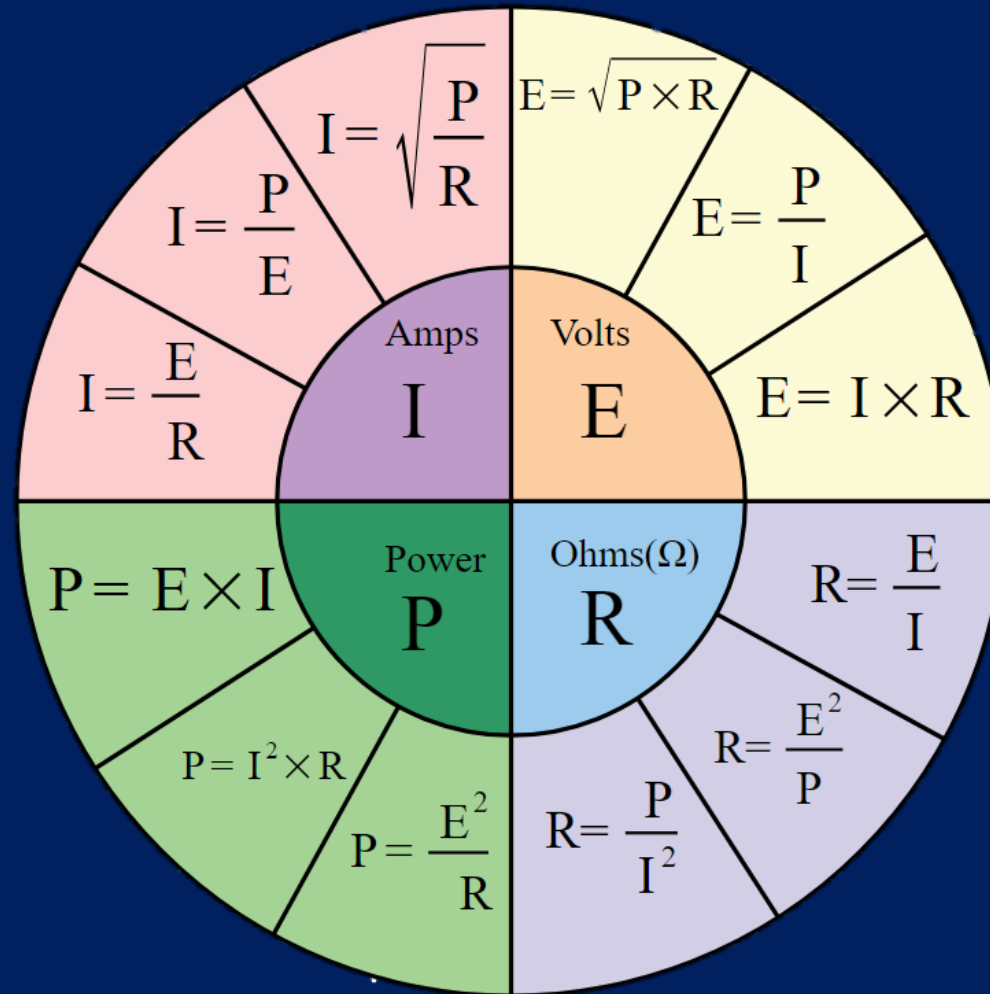


# Kirchoff's Law

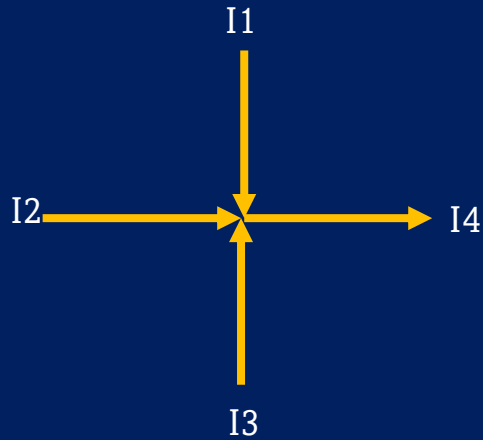

$$\text{KCL} : I_{in} = I_{out}$$

$$\text{KCL} : I_1 + I_2 + I_3 = I_4$$

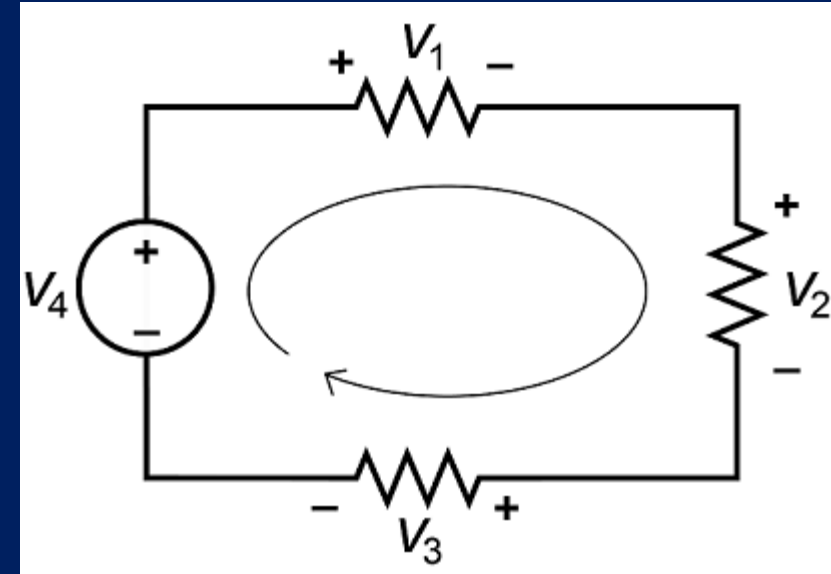The sum of the current entering any point is equal to the sum of the current leaving the same point



$$\text{KVL} : \sum V = 0$$

$$\text{KVL} : V_1 + V_2 + V_3 = V_4$$

The sum of the voltage in any close loop is equal to zero


# Total Resistance

## Series connection




$$R_t = R_1 + R_2 + \dots + R_n$$

## Parallel connection

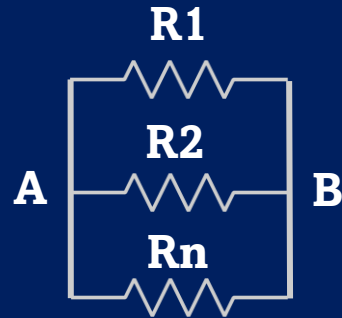


$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

## 2 Resistor connected in parallel

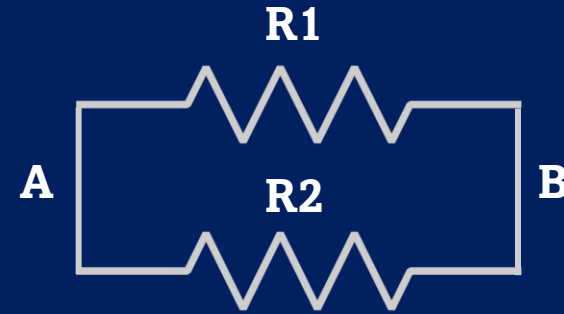

$$R_t = \frac{R_1 \times R_2}{R_1 + R_2}$$

## What if...

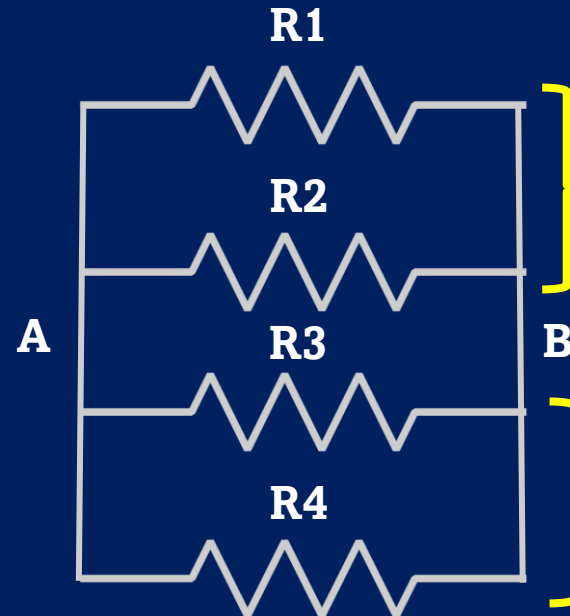


$$R_a = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_b = \frac{R_3 \times R_4}{R_3 + R_4}$$

$$R_t = \frac{R_a \times R_b}{R_a + R_b}$$

# Voltage divider

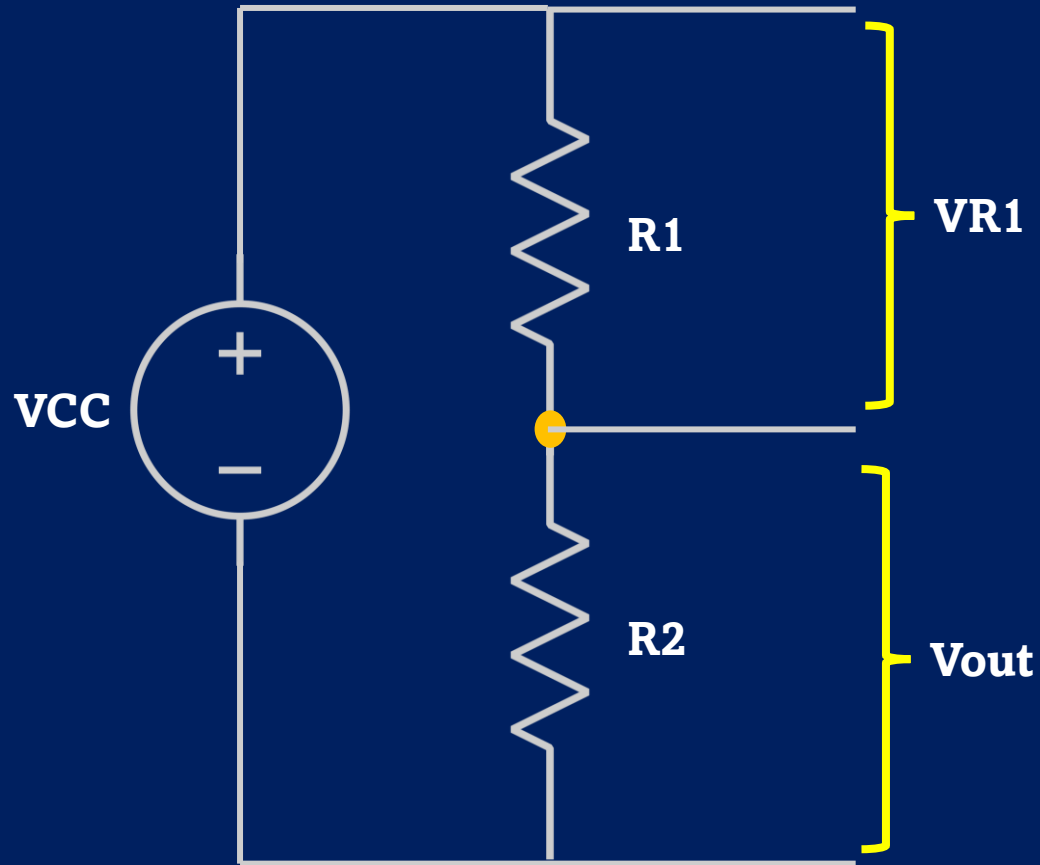



The voltage is depends on it's own resistance

$$V_{R1} = V_{CC} \times \left( \frac{R_1}{R_1 + R_2} \right)$$


$$V_{out} = V_{CC} \times \left( \frac{R_2}{R_1 + R_2} \right)$$



# The Light Emitting Diode

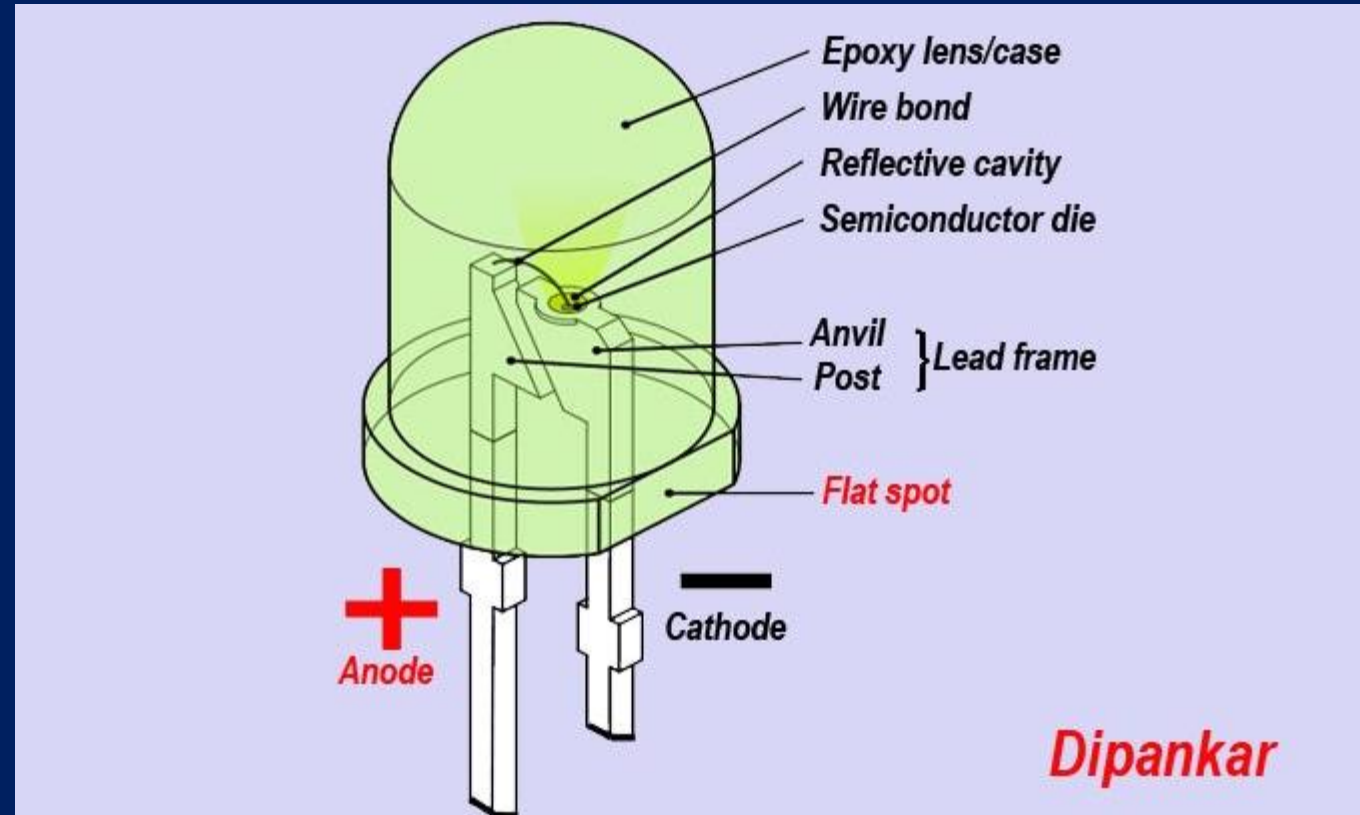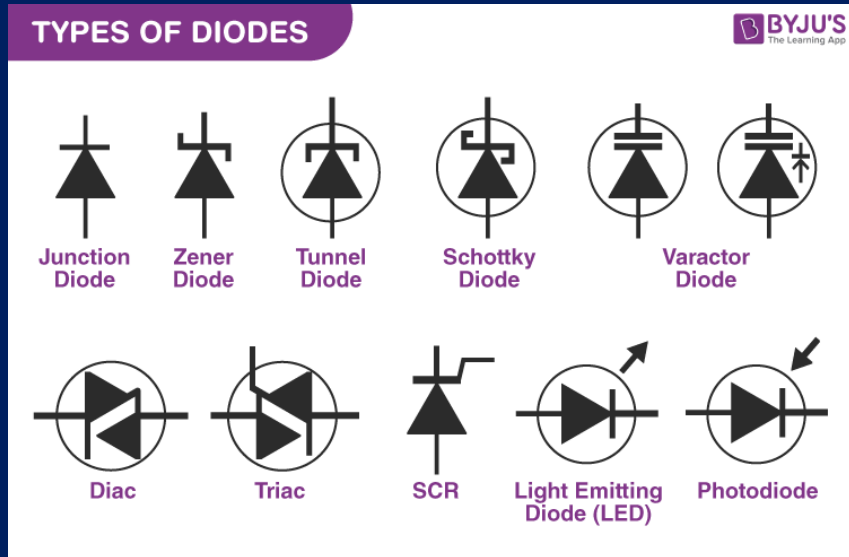

# The pulldown resistor

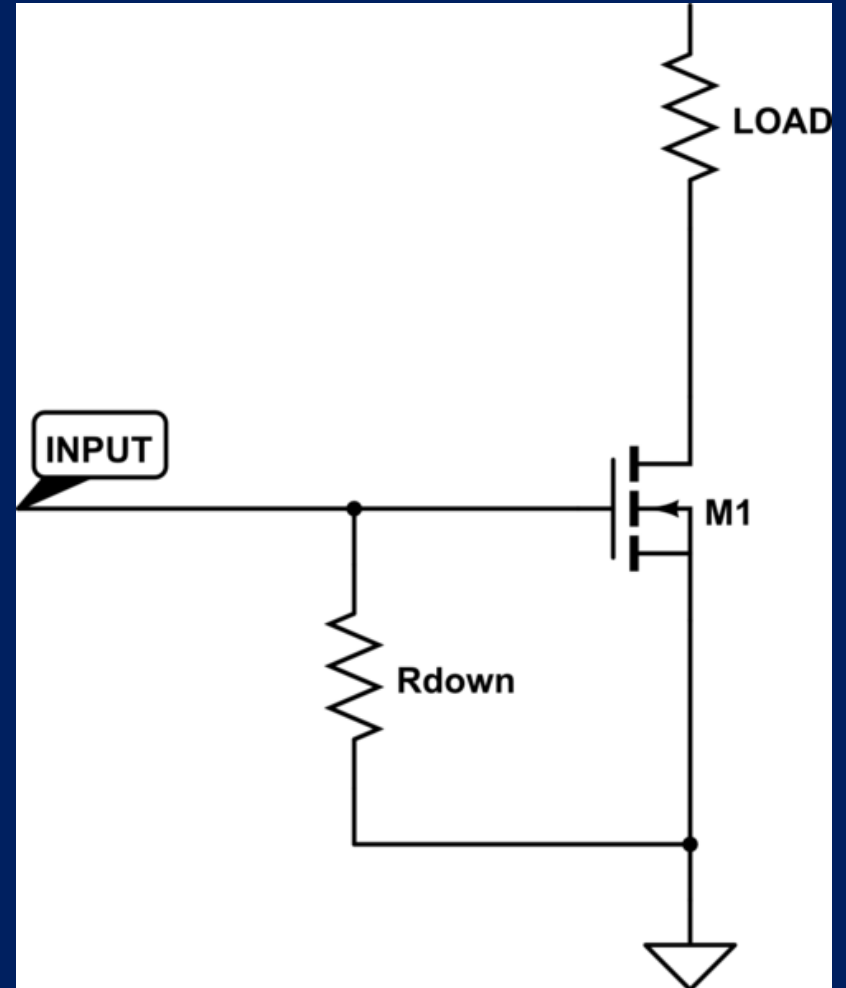

# Bread board

